

## **PRISM WORLD**

Std.: 9 (English) Science 1 Marks: 20 Time: 1 hour Date: Chapter: 3 Q.1 A) Choose the correct alternative and rewrite the sentence (1) Which particles are responsible for flow of current in metallic conductors? a. protons b. electrons d. none of the above c. neutrons B) Answer the following questions. (2) 1) Find co-related terms Ammeter: current::.....: Potential difference. Find the odd man out: Potential difference, Electric current, Resistance, The coulomb Q.2 A) Give scientific reasons (Any one) (2) Metals are good conductors of electricity. 1) 2) While handling an electrical device, hands should be dry. B) Answer the following questions. (Any two) (4) 1) Write short notes Colours of your Dreams 1) 'Electric potential difference'. 2) Distinguish between OHMIC Conductor and Non-OHMIC Conductor 3) Two resistances of 4  $\Omega$  and 6  $\Omega$  are connected in parallel. Find their equivalent resistance. Q.3 Answer the following questions. (Any two) (6) 1) What should be done if a person gets an electric shock? Why our body can conduct electricity? 2) The resistance of a 1m long nichrome wire is 6  $\Omega$  If we reduce the length of the wire to 70 cm. What will be the resistance. 3) The following figures show conducting wires of different lengths. Answer the questions. a. Which wire has greater resistance? Why? b. Write the expression for resistivity.

c. How will you prove that the unit of resistivity is  $\Omega$  m?

## Q.4 Answer the following questions. (Any one)

(5)

1) The given figure shows some electrical appliances connected in a circuit in a house. Answer the following questions.



- a. By which method are the appliances connected?
- b. What must be the potential difference across individual appliances?
- c. Will the current passing through each appliance be the same? Justify your answer.
- d. Why are domestic appliances connected in this way?
- e. If the TV stops working, will the other appliances also stop working? Explain your answer.
- 2) Derive the expression for the resisters connected in series combination.

